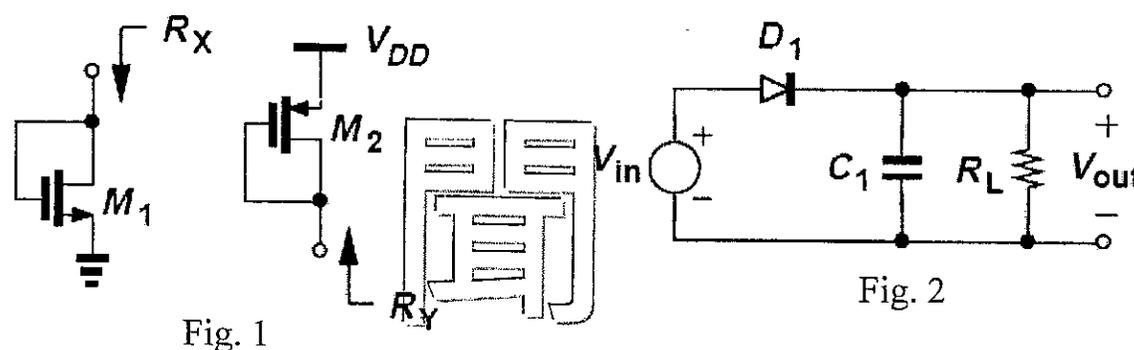



1. 依次序作答，只要標明題號，不必抄題。
2. 答案必須寫在答案卷上，否則不予計分。
3. 限用藍、黑色筆作答；試題須隨卷繳回。

1. Please explain the following terms:
 - (a) Electrons (電子) & holes (電洞) (5 points)
 - (b) Depletion region (空乏區) of a diode. (5 points)
 - (c) Junction capacitance (接面電容) of a diode (5 points)
 - (d) Body effect in MOSFET. (5 points)
 - (e) CMOS technology. (5 points)
2. For the configurations shown in Fig. 1, determine the small-signal resistances R_X and R_Y . Assume $\lambda \neq 0$ (i.e. output resistance r_o is not negligible). (10 points)



3. (a) For the half-wave rectifier shown in Fig. 2, plot the output waveform for different values of smoothing capacitor C_1 . (10 points)
- (b) Describe the advantages of a full-wave rectifier when compared with a half-wave rectifier. (5 points)

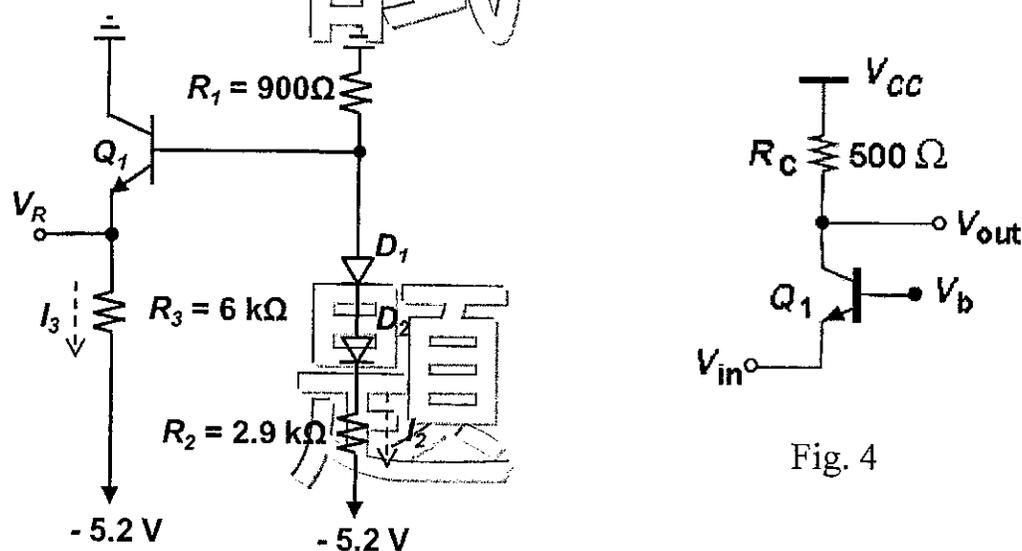4. In Fig. 3, calculate the values of I_2 , I_3 and V_R . Assume that the voltage drop across the diodes (D_1, D_2) and V_{BE} of Q_1 is 0.7V. Neglect the base current of Q_1 . (10 points)



5. In Fig. 4, Q_1 has $\beta = 80$, $V_A = 15$ V, and is biased at $I_C = 2.5$ mA. Assume $V_T = 25$ mV. Calculate its voltage gain (A_v), input resistance (R_{in}), and output resistance (R_{out}). (10 points)

科目：電子學

適用：電機系三

考生注意：

1. 依次序作答，只要標明題號，不必抄題。
2. 答案必須寫在答案卷上，否則不予計分。
3. 限用藍、黑色筆作答；試題須隨卷繳回。

本試題
共 2 頁
第 2 頁

編號：731

6. In Fig. 5, assume M_1 is at saturation and has $(W/L)_1 = 50$, $\mu_n C_{ox} = 50 \mu\text{A}/\text{V}^2$, $V_{TH} = 0.5\text{V}$, $\lambda = \gamma = 0$. $V_{DD} = 3\text{V}$, $I_{out} = 200 \mu\text{A}$.

(a) Determine R_1/R_2 . (5 points)

(b) Calculate the sensitivity of I_{out} to V_{DD} , defined as $\partial I_{out}/\partial V_{DD}$ and normalized to I_{out} . (5 points)

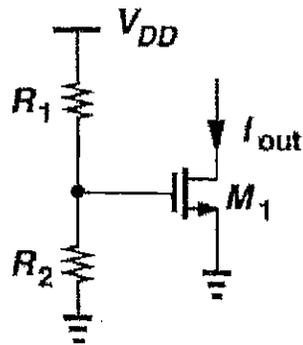


Fig. 5

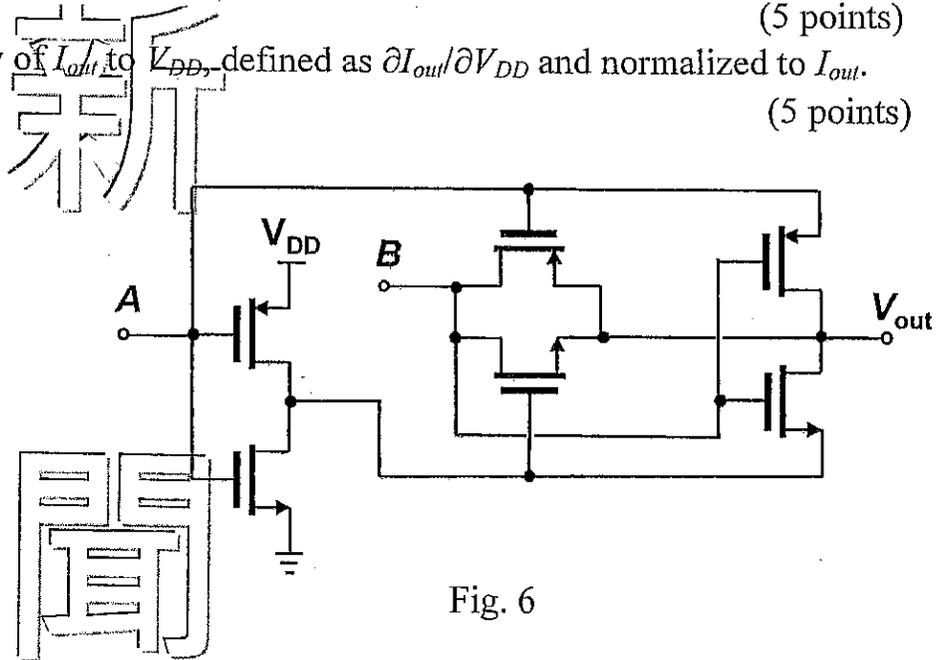


Fig. 6

7. In Fig. 6, A and B are two logic inputs. What is the logic function of V_{out} ? (5 points)

8. In Fig. 7, the MOSFETs have their geometry size as labelled, and V_{DD} is 5V. Calculate the voltage values of V_1 and V_2 . (5 points)

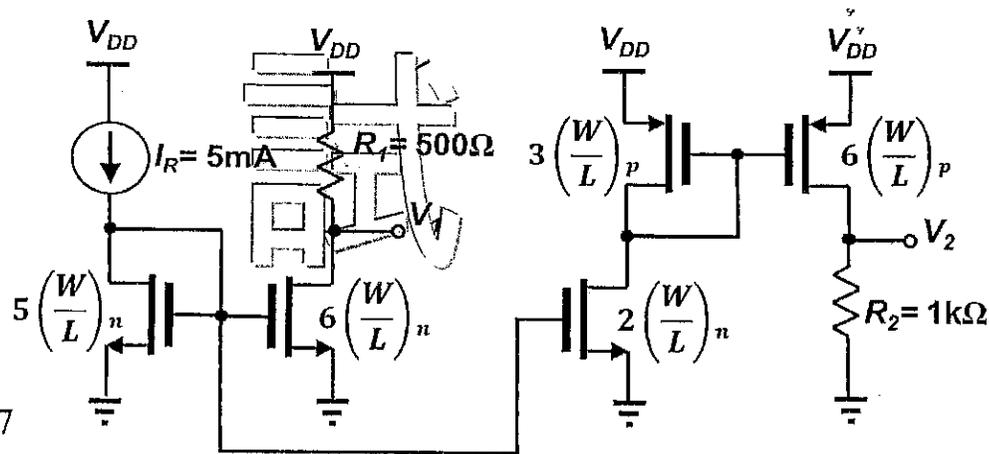


Fig. 7

9. In Fig. 8, assume the operational amplifier is ideal.

(a) Derive the transfer function, $H(s) = V_{out}/V_{in}$. (5 points)

(b) What type of filter it is? (5 points)

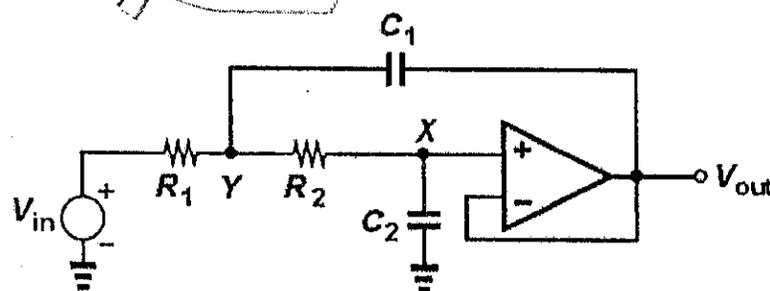


Fig. 8