

科目：電子學甲 適用：電機系(電子組)

編號：462

考生注意：

1. 依次序作答，只要標明題號，不必抄題。
2. 答案必須寫在答案卷上，否則不予計分。
3. 限用藍、黑色筆作答；試題須隨卷繳回。

本 試 題

共 2 頁

第 1 頁

1. A mobile phone receives a signal level of  $10 \mu\text{V}$ , but it must deliver a swing of  $10 \text{ mV}$  to the speaker that reproduces the voice. Calculate the required voltage gain in decibels (dBs). (10 points)

2. Prove the "small-signal resistance" ( $r_d$ ) of a diode at forward bias is equal to  $r_d = \frac{V_T}{I_D}$ . (10 points)

3. Compute the voltage gain, input impedance, and output impedance of the circuit depicted in Fig. 1. Assume a very large value for  $C_1$ . (20 points)


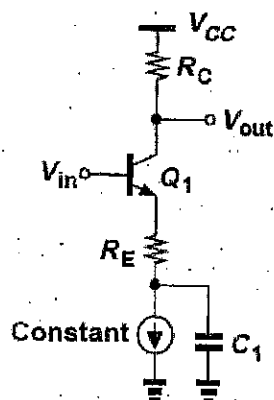


Fig. 1

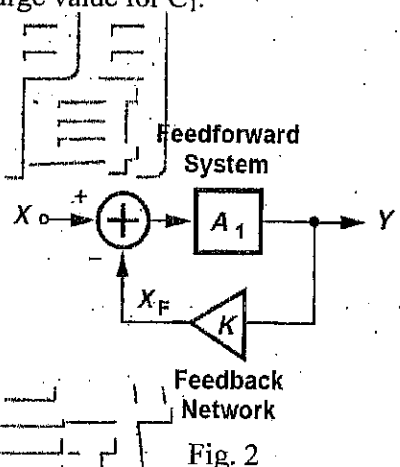

4. Fig. 2 shows a general feedback system. Suppose the amplifier  $A_1(s)$  can be represented as follows:  $A_1(s) = \frac{A_0}{1 + \frac{s}{\omega_0}}$ , in which  $A_0$  denotes the low-frequency gain

and  $\omega_0$  the  $-3\text{-dB}$  bandwidth. Prove the closed-loop system exhibits:

(a) Closed-loop gain  $= \frac{A_0}{1 + KA_0}$ . (10 points)

(b) Closed-loop bandwidth  $= (1 + KA_0)\omega_0$ . (10 points)

科目：電子學甲 適用：電機系(電子組)

編號：462

考生注意：

1. 依次序作答，只要標明題號，不必抄題。
2. 答案必須寫在答案卷上，否則不予計分。
3. 限用藍、黑色筆作答；試題須隨卷繳回。

本試題

共 2 頁

第 2 頁

5. Determine the transfer function and frequency response of the common-source stage shown in Fig. 3. (20 points)

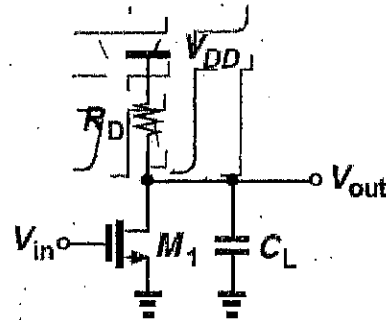


Fig. 3

6. For the KHN bi-quad in Fig. 4,
- (a) Prove  $V_{out}/V_{in}$  is a second-order high-pass function. (8 points)
  - (b) Prove  $V_X/V_{in}$  is a second-order band-pass function. (6 points)
  - (c) Prove  $V_Y/V_{in}$  is a second-order low-pass function. (6 points)

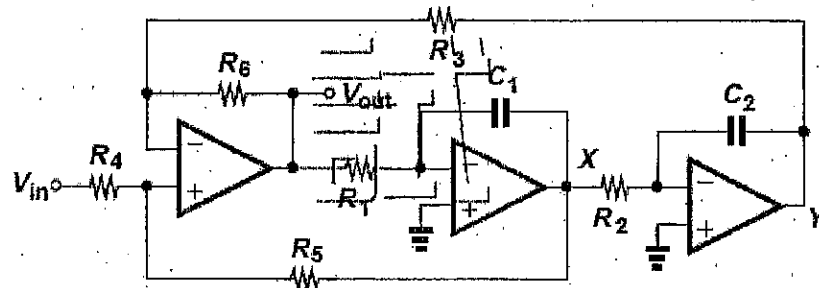


Fig. 4

題