

科目：電子學

適用：電機系三

考生注意：

1. 依次序作答，只要標明題號，不必抄題。
2. 答案必須寫在答案卷上，否則不予計分。
3. 限用藍、黑色筆作答；試題須隨卷繳回。

本 試 題  
共 2 頁  
第 1 頁

編號：731

1. In Fig. 1,  $Q_1$  has  $\beta = 100$ ,  $V_A = 13$  V, and is biased at  $V_{BE} = 0.7$  V,  $I_C = 1$  mA. Also  $V_T = 26$  mV,  $V_{CC} = 3$  V,  $V_b = 1$  V.
- (a) Calculate the DC voltages at  $V_{in}$  and  $V_{out}$  nodes. (4 points)
  - (b) Calculate the voltage gain ( $A_v$ ), input resistance ( $R_{in}$ ), and output resistance ( $R_{out}$ ). (6 points)

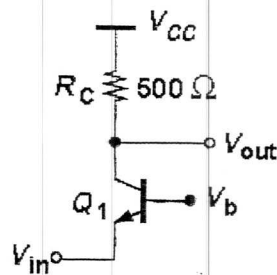


Fig. 1

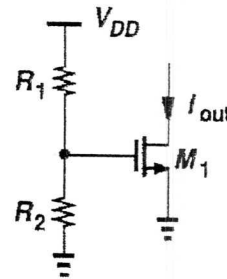


Fig. 2

2. In Fig. 2, assume  $M_1$  is biased at saturation and has  $(W/L)_1 = 100$ ,  $\mu_n C_{ox} = 100 \mu\text{A/V}^2$ ,  $V_{TH} = 0.8$  V,  $\lambda = \gamma = 0$ .  $V_{DD} = 3$  V,  $I_{out} = 200 \mu\text{A}$ .
- (a) Find  $V_{GS}$  of  $M_1$ . (5 points)
  - (b) Determine  $R_1/R_2$ . (5 points)
3. In Fig. 3, find  $V_{GS}$  and  $I_D$  of  $M_1$ .  $\mu_n C_{ox} = 100 \mu\text{A/V}^2$ ,  $V_{TH} = 0.5$  V,  $\lambda = 0$ . (10 points)

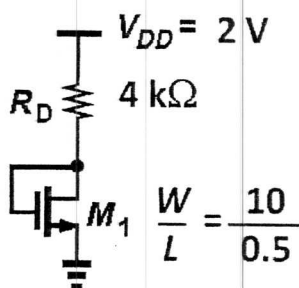


Fig. 3

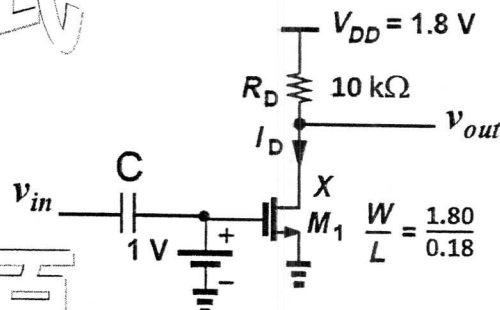


Fig. 4

4. For the circuit shown in Fig. 4,  $M_1$  has  $\mu_n C_{ox} = 80 \mu\text{A/V}^2$ ,  $V_{TH} = 0.5$  V,  $\lambda = 0.1 \text{ V}^{-1}$ .
- (a) Find the current ( $I_D$ ), transconductance ( $g_m$ ) and output resistance ( $r_o$ ) of  $M_1$ . (6 points)
  - (b) If  $C$  is large enough, find the voltage gain  $A_v (= v_{in}/v_{out})$ . (4 points)
  - (c) What is the maximum value of  $R_D$  such that  $M_1$  stays at saturation? (5 points)

科目：電子學

適用：電機系三

考生注意：

1. 依次序作答，只要標明題號，不必抄題。
2. 答案必須寫在答案卷上，否則不予計分。
3. 限用藍、黑色筆作答；試題須隨卷繳回。

本 試 題

共 2 頁

第 2 頁

編號：731

5. In Fig. 5, the MOSFETs have their geometry size as labelled, and  $V_{DD}$  is 5V. Calculate the voltage values of  $V_1$  and  $V_2$ . (5 points)

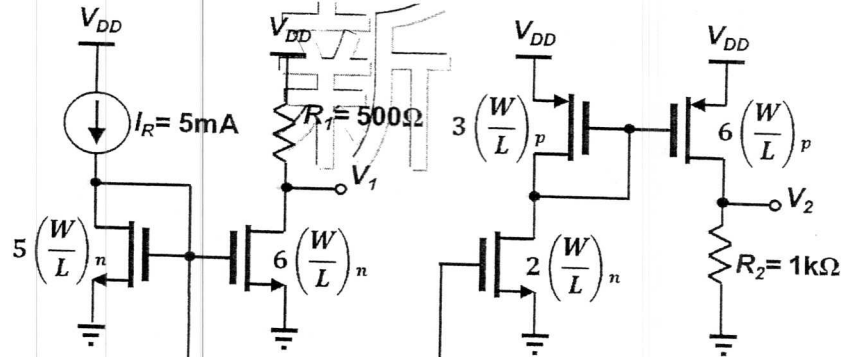


Fig. 5

6. Please define the following terms. (5 points)
- (a) Depletion region (空乏區) of a diode (二極體) (5 points)
  - (b) Junction capacitance (接面電容) of a diode (5 points)
  - (c) Drift current (飄移電流) (5 points)
  - (d) Diffusion current (擴散電流) (5 points)
  - (e) N-type doping (N-型摻質) (5 points)
7. Fig. 6 shows the small-signal model including channel-length modulation of a MOSFET. Prove output resistance  $r_o$  and transconductance  $g_m$  can be represented as follows: (5 points)
- (a)  $r_o \approx \frac{1}{\lambda I_D}$  (5 points)
  - (b)  $g_m = \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})$  (5 points)
  - (c)  $g_m = \sqrt{2\mu_n C_{ox} \frac{W}{L} I_D}$  (5 points)

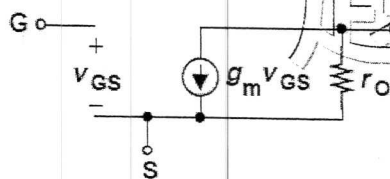


Fig. 6

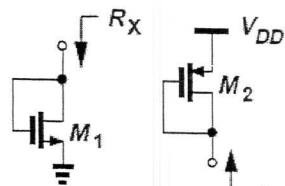


Fig. 7

8. For the configurations shown in Fig. 7 determine the small-signal resistances  $R_X$  and  $R_Y$ . Assume  $\lambda \neq 0$ . (10 points)