

科目：電子學乙 適用：電機系(系統組)

編號：473

考生注意：

1. 依次序作答，只要標明題號，不必抄題。
2. 答案必須寫在答案卷上，否則不予計分。
3. 限用藍、黑色筆作答；試題須隨卷繳回。

 本試題  
共 2 頁  
第 / 頁

1. Fill the blanks with either 0 or  $\infty$ . (a) An ideal current amplifier has its input resistance,  $R_{in} =$  ①, and output resistance,  $R_{out} =$  ②. (b) An ideal operational amplifier would have ③ voltage gain, ④ input impedance, ⑤ output impedance, and ⑥ bandwidth. [12 pts, each blank 2 pts]
2. For a saturation n-type MOSFET, (a) how does its transconductance,  $g_m$ , relate to its threshold voltage ( $V_T$ ), applied gate-source voltage ( $V_{GS}$ ), aspect ratio ( $W/L$ ), and drain current ( $I_D$ )? [7 pts] (b) How does  $g_m$  change for the following conditions? Fill the blanks with *increase*, *decrease* or *not change*. [8 pts, each blank 2 pts]
  - (a)  $W/L$  is doubled but  $I_D$  remains constant.  $g_m$  will ①.
  - (b)  $V_{GS} - V_{TH}$  is doubled but  $I_D$  remains constant.  $g_m$  will ②.
  - (c)  $I_D$  is doubled but  $W/L$  remains constant.  $g_m$  will ③.
  - (d)  $I_D$  is doubled but  $V_{GS} - V_{TH}$  remains constant.  $g_m$  will ④.
3. For a MOSFET,  $M_1$ , four bias cases are as shown in Fig. 1. Assume the threshold voltage,  $V_T$ , of  $M_1$  is 0.5V. What is its operation mode for each bias case? Answer each with *cutoff*, *linear*, or *saturation*. [8 pts, each answer 2 pts]

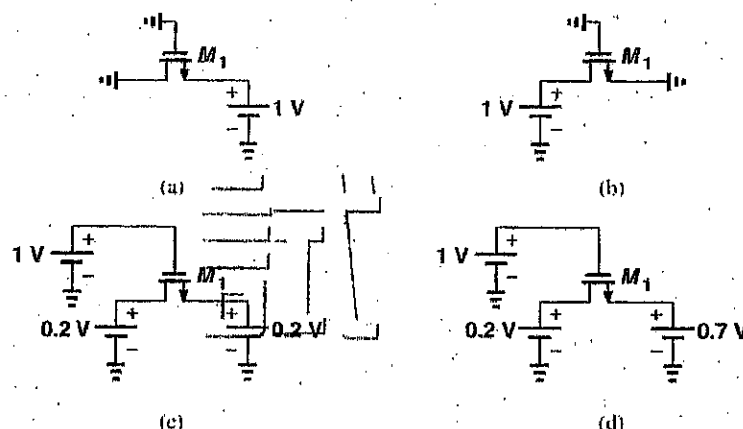


Fig. 1

4. In Fig. 2,  $R_1 = R_2$ . Assume  $D_1$  behaves as an ideal switch with a turn on voltage of 0.5V. Derive or plot its input/output characteristic. [5 pts]

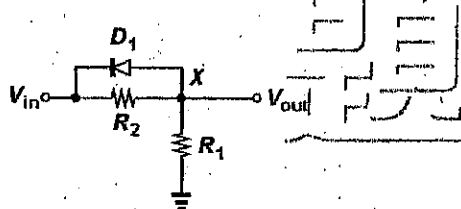


Fig. 2

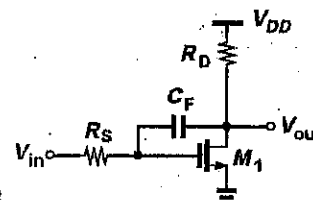


Fig. 3

5. Estimate the poles of the circuit shown in Fig. 3 using Miller's theorem. Assume  $M_1$  has a transconductance of  $g_m$  and  $\lambda = 0$ . [10 pts]

科目：電子學乙 適用：電機系(系統組)

編號：473

考生注意：

1. 依次序作答，只要標明題號，不必抄題。
2. 答案必須寫在答案卷上，否則不予計分。
3. 限用藍、黑色筆作答；試題須隨卷繳回。

本試題

共 2 頁

第 2 頁

6. Assume the op amps in Fig. 4 are ideal. (a) Determine  $Z_{in}$ . [5 pts] (b) What type of component the circuit simulated? [5 pts]

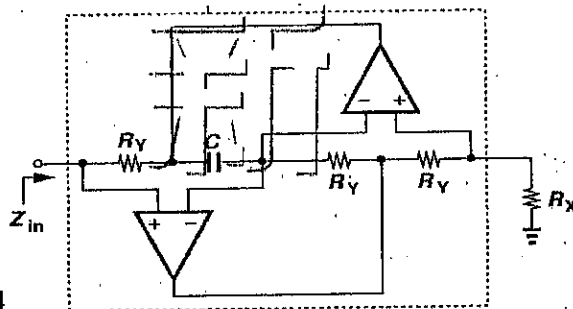


Fig. 4

7. Assume the op amp in Fig. 5 is ideal. (a) Derive the transfer function,  $V_{out}/V_{in}(s)$ . [5 pts] (b) What type of filter the circuit realized? [5 pts]

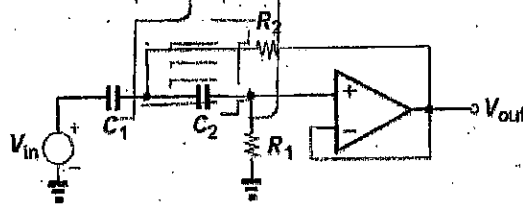


Fig. 5

8. For the circuit shown in Fig. 6, (a) what is its feedback topology? [5 pts] (b) Determine the voltage gain,  $V_{out}/V_{in}$ , if  $A_1 = \infty$ . [5 pts] (c) Repeat problem (b) if  $A_1 \neq \infty$ . [5 pts]

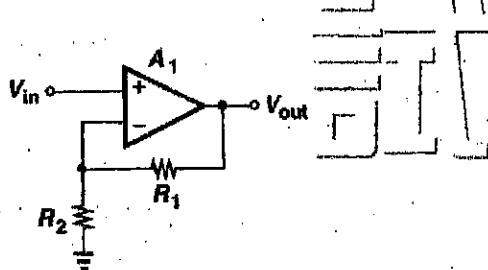


Fig. 6

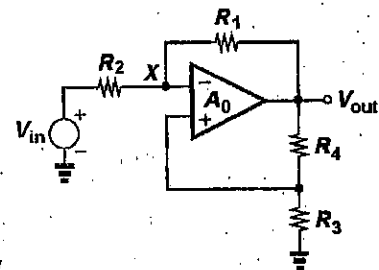


Fig. 7

9. Determine the voltage gain,  $V_{out}/V_{in}$ , of the circuit shown in Fig. 7 if  $R_1 = R_4 = 10 \text{ K}\Omega$ ,  $R_2 = R_3 = 1 \text{ K}\Omega$ , and  $A_0 = \infty$ . [10 pts]

10. Determine the current values of  $I_1$  and  $I_2$  of the circuit shown in Fig. 8. [5 pts]

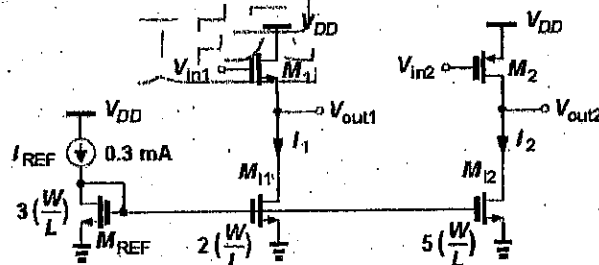


Fig. 8