

科目：電子學 適用：應光系

編號：423

考生注意：

1. 依次序作答，只要標明題號，不必抄題。
2. 答案必須寫在答案卷上，否則不予計分。
3. 限用藍、黑色筆作答；試題須隨卷繳回。


本試題

共 2 頁


第 / 頁

1. (a) What is the approximation electron concentration of the N-type Si in terms of the impurity concentration? (4 %)
- (b) What is the approximation hole concentration of the P-type Si in terms of the impurity concentration? (4 %)
- (c) How is the built-in potential barrier in a pn junction formed? (4 %)
- (d) What is Schottky barrier diode? How does it differ from a pn junction diode? (4 %)
- (e) Describe a simple full-wave diode rectifier circuit. Assume the input signal is sinusoidal, sketch the output voltage versus time. (4 %)

2. Design a diode clamper to generate a steady-state output voltage v_o from the input signal v_i shown.

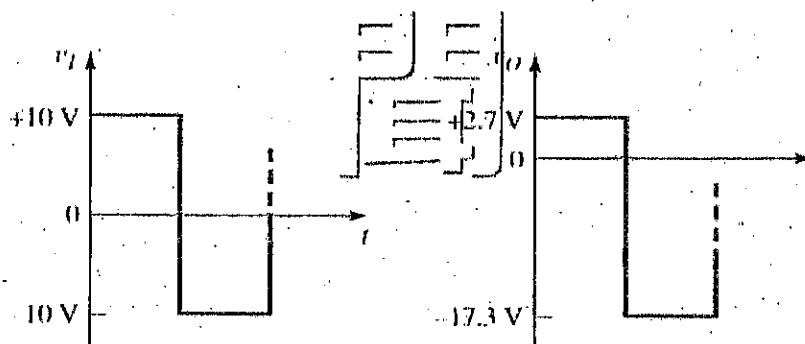(a) Assume the cut-in voltage of the diode $V_f = 0$. (10%)(b) Assume the cut-in voltage of the diode $V_f = 0.7$ V. (10%)

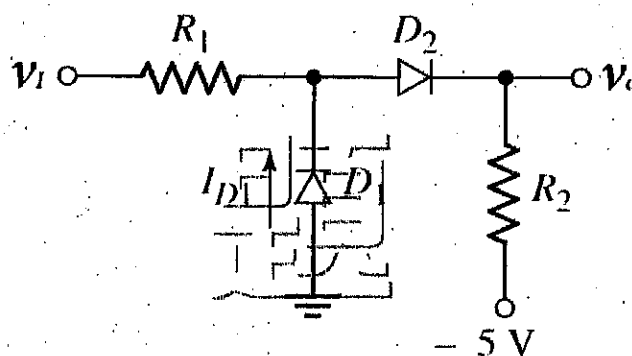3. Assume each diode cut-in voltage is $V_f = 0$, $R_1 = 10$ k Ω and $R_2 = 5$ k Ω . Plot the voltage transfer characteristics v_o versus v_i . Indicate the breakpoints and give the state of each diode in the various region of the plot. (20%)



科目：電子學 適用：應光系

編號：423

考生注意：

1. 依次序作答，只要標明題號，不必抄題。
2. 答案必須寫在答案卷上，否則不予計分。
3. 限用藍、黑色筆作答；試題須隨卷繳回。

本試題


共 2 頁

第 2 頁

4. For the transistor in the circuit shown, assume $\beta = 150$, $V_A = \infty$.

(a) Determine R_1 and R_2 to obtain a bias-stable circuit with the Q-point in the center of the load line. (10%)

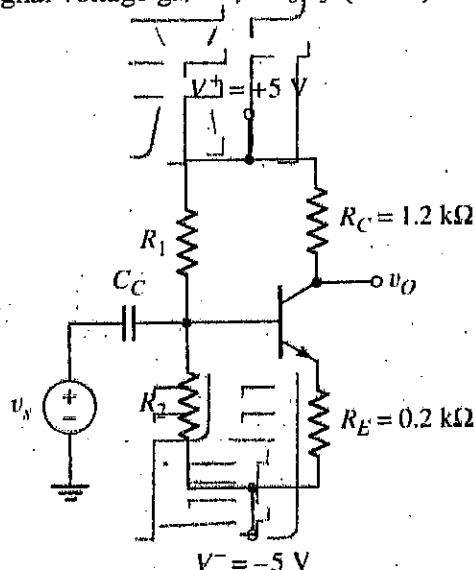(b) Determine the small-signal voltage gain $A_v = v_o/v_s$. (10%)



5. The small-signal parameters of the transistor shown are $g_m = 2 \text{ mA/V}$ and $r_o = \infty$.

(a) What is the value of R_D if the voltage gain is found to be $A_v = V_o/V_i = -1.5$ with $R_S = 0$. (10%)

(b) What is the value of R_S if the voltage gain is reduced to $A_v = -5$ with the R_D found in (a). (10%)

