

科目：電子學

適用：電機系

編號：351


考生注意：

1. 依次序作答，只要標明題號，不必抄題。
2. 答案必須寫在答案卷上，否則不予計分。
3. 限用藍、黑色筆作答；試題須隨卷繳回。

本 試 題  
共 3 頁  
第 / 頁

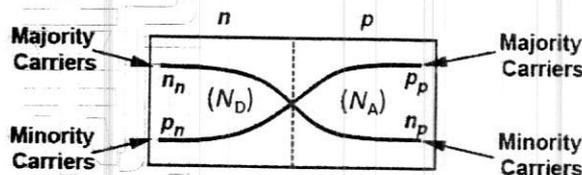1. In Fig. 1, a silicon *pn* junction has doping of  $N_A = 5 \times 10^{15} \text{ cm}^{-3}$  and  $N_D = 2 \times 10^{16} \text{ cm}^{-3}$ . Assume the number of electrons per unit volume for pure silicon is  $n_i = 10^{10} \text{ cm}^{-3}$ .
  - (a) Determine the electron and hole densities in both sides of junction. [5%]
  - (b) Determine the built-in potential,  $V_B$ , at room temperature. [5%]

Use  $V_B = 25 \times \ln \frac{N_A \cdot N_D}{n_i^2} \text{ mV}$ ,  $\ln 10 = 2.3$



$n_n$ : Concentration of electrons on n side  
 $p_n$ : Concentration of holes on n side  
 $p_p$ : Concentration of holes on p side  
 $n_p$ : Concentration of electrons on p side

Fig. 1

2. In the circuit of Fig. 2, each input can assume a value of either zero or  $V_{DD} = 5 \text{ V}$ . Determine the response observed at the output. Assume the diode is ideal. [5%]

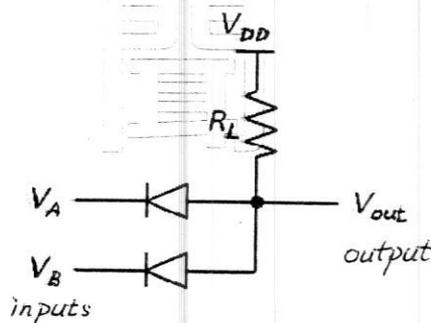


Fig. 2

3. In the circuit of Fig. 3,  $Q_1$  has  $I_S = 5 \times 10^{-16} \text{ A}$ , and  $\beta = 100$ ,  $V_A = 10 \text{ V}$ .
  - (a) Determine the terminal currents ( $I_B$ ,  $I_C$ , and  $I_E$ ) of  $Q_1$  and verify operation in the forward active region. [5%]
  - (b) Derive its small signal parameters,  $g_m$ ,  $r_\pi$ , and  $r_o$ . [5%]

$I_C = I_S \cdot e^{\frac{V_{BE}}{V_T}}$ ,  $V_T = 25 \text{ mV}$ , and  $e^{30} \approx 10^{13}$ .  $g_m = \frac{dI_C}{dV_{BE}}$ ,  $r_\pi = \frac{dV_{BE}}{dI_B}$ ,  $r_o = \frac{dV_{CE}}{dI_C}$

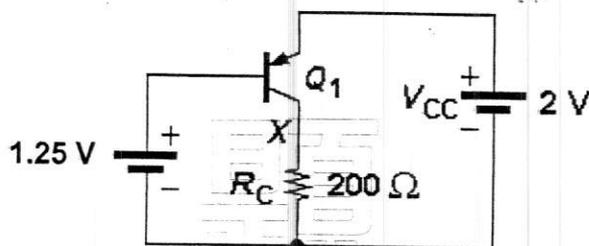


Fig. 3

科目：電子學

適用：電機系

考生注意：

1. 依次序作答，只要標明題號，不必抄題。
2. 答案必須寫在答案卷上，否則不予計分。
3. 限用藍、黑色筆作答；試題須隨卷繳回。

本 試 題  
共 3 頁  
第 2 頁

編號：351

4. In Fig. 4,  $M_1$  has  $\mu_n C_{ox} = 100 \mu\text{A}/\text{V}^2$ ,  $V_{TH} = 0.5 \text{ V}$ ,  $\lambda = 0.1 \text{ V}^{-1}$ , and  $(W/L)_1 = 20$ , and  $V_{DD} = 2.5 \text{ V}$ ,  $R_D = 800 \Omega$ ,  $R_G = 20 \text{ k}\Omega$ ,  $R_S = 200 \Omega$ .

- (a) Calculate the drain current,  $I_D$ . [5%]  
 (b) Find its small signal parameters,  $g_m$  and  $r_o$ . [5%]

$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^2 \quad g_m = \sqrt{2 \mu_n C_{ox} \frac{W}{L} I_D}$$

$$r_o = \frac{1}{\lambda I_D}$$

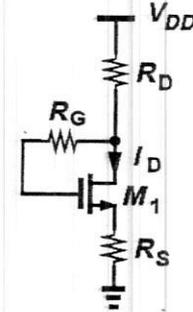


Fig. 4

5. In Fig. 5, find  $V_1$  and  $V_2$ . [10%]

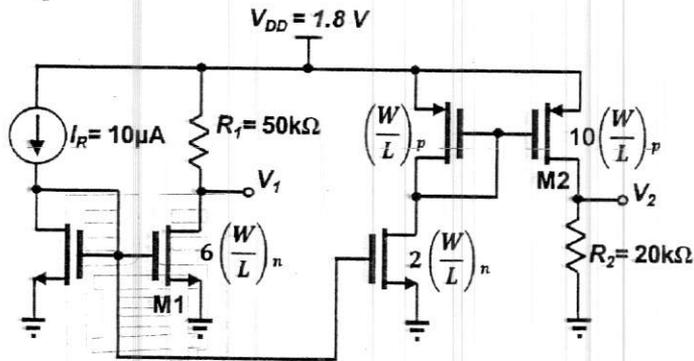


Fig. 5

6. Determine the closed-loop gain of the circuit in Fig. 6,

- (a) if  $A_0 = \infty$ . [5%]  
 (b) if  $A_0 \neq \infty$ , and  $R_1 = R_4$ ,  $R_2 = R_3$ . [5%]

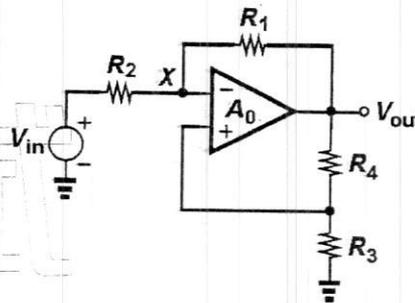


Fig. 6

7. In Fig. 7, derive  $H(s) = V_{out}/V_{in}$  if the Op-Amp is ideal. [10%]

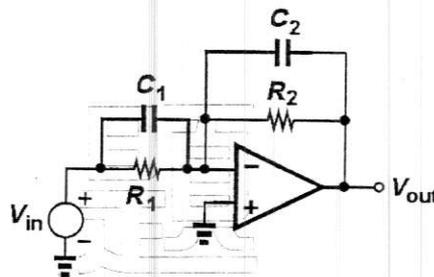


Fig. 7

8. Draw the Bode plot of magnitude and phase for the transfer function below. [10%]

$$H(s) = \frac{10^4 s}{(s^2 + 110s + 1000)}$$

No Fig. 8

9. The circuit shown in Fig. 9 has a voltage gain of 8, and input impedance ( $R_{in}$ ) of 24 k $\Omega$ .  $V_{DD} = 2.5$  V,  $R_G = 0$ ,  $R_S = 200$   $\Omega$ ,  $R_D = 400$   $\Omega$ , a voltage drop of 400 mV across  $R_S$ , and both  $C_1$  and  $C_2$  are large enough.

(a) Find  $g_m$ ,  $I_D$ , and  $V_{GS}$  of  $M_1$ . [10%]

(b) Find  $R_1$  and  $R_2$ . [10%]

(c) Find the DC voltage at  $V_{out}$  node, and the total power consumption. [5%]

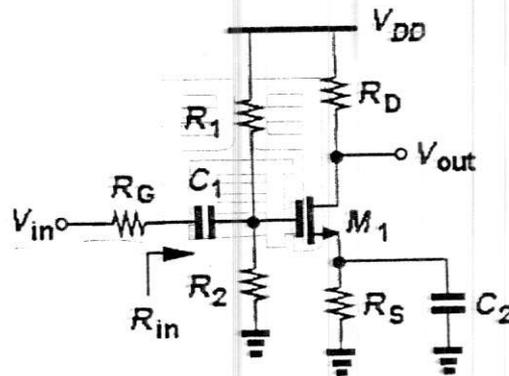


Fig. 9