 



考生注意: 1. 依次序作答, 只要標明題號, 不必抄題。  
 2. 答案必須寫在答案卷上, 否則不予計分, 並限以藍黑色筆作答。  
 3. 試題隨卷繳回。(餘請詳閱試場規則)

1. The circuit shown below is an NMOS amplifier with enhancement load. Assume that the channel-length-modulation effect and body effect can be neglected, please show that the voltage gain of the amplifier can be expressed as:

$$A_v = -\frac{(W/L)_1}{(W/L)_2}$$



 2. If the BJT in the circuit shown below has been biased in its forward active region, please find the expression for the output voltage  $V_o$  in terms of the two input signals  $V_{i1}$  and  $V_{i2}$ . (15%)




3. (a) Please plot the minority carrier distribution in a PN junction under forward bias and reverse bias. (10%)  
 (b) Explain why there exists a minority carrier storage time in a PN junction that is driven from the forward-state to the reverse state. (10%)
4. (a) Calculate the dc offset voltage ( $V_{OS}$ ) of the MOS differential pair shown below caused by mismatch in threshold voltage  $V_t$ . (16%)  
 (b) Give the other two factors that contribute to the dc offset voltage of the

考生注意: 1. 依次序作答, 只要標明題號, 不必抄題。


2. 答案必須寫在答案卷上, 否則不予計分, 並限以藍黑色筆作答。

3. 試題隨卷繳回。(餘請詳閱試場規則)

MOS differential pair. (4%)

 

 5. For the circuit shown below, please determine its voltage transfer characteristic. (15%)



6. (a) The open-loop gain of an amplifier is given by  $A(s) = \frac{1}{s^2 + 3}$ . Determine the close-loop step response of the amplifier. Is the amplifier stable or unstable? (9%) (Assuming  $\beta(s) = 1$ )
- (b) Define the phase margin and gain-margin of a feedback amplifier. (6%)