

考生注意: 1. 依次序作答, 只要標明題號, 不必抄題。

2. 答案必須寫在答案卷上, 否則不予計分, 並限以藍黑色筆作答。

3. 試題隨卷繳回。(餘詳詳閱試場規則)

1. (15%) Two diodes are connected in parallel as shown in Fig. 1. Diode A has a reverse saturation current of 1.0×10^{-7} A, while diode B has a reverse saturation current of 1.0×10^{-8} A at 300 K. Calculate the current in each diode.

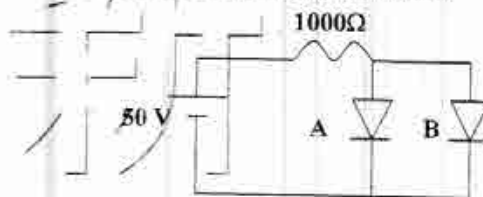


Fig. 1

2. (20%) One curve of an n-channel MOSFET is characterized by following parameters: $I_d(\text{sat}) = 2 \times 10^{-4}$ A, $V_{ds}(\text{sat}) = 4$ V and $V_T = 0.8$ V.
- What is the gate voltage?
 - What is the value of conduction parameters K_n , if $I_d(\text{sat}) = K_n (V_{gs} - V_T)^2$?
 - If $V_g = 2$ V and $V_{ds} = 2$ V determine I_d ?
 - If $V_g = 3$ V and $V_{ds} = 1$ V determine I_d ?

3. (15%) Consider a uniformly doped silicon pn junction with doping concentrations $N_a = 5 \times 10^{17}$ and $N_d = 10^{17} \text{ cm}^{-3}$. The junction area is 10^{-4} cm^2 and a reverse-bias of 5 V is applied. Calculate

- The junction built-in voltage
- Width of depletion region
- Total junction capacitance.

4. Fig. 2 shows a cascode amplifier designed using bipolar transistor. Suppose $V_{\pi 1} \approx V_{\pi 2}$, in which $V_{\pi 1}$ and $V_{\pi 2}$ represents the voltage across the base-emitter capacitances $C_{\pi 1}$ and $C_{\pi 2}$, respectively, of transistors Q_1 and Q_2 .

- (a) Prove the mid-band gain is given by $A_M = \frac{V_o}{V_s} \approx -g_{m2} R_L \frac{r_{\pi 1}}{r_{\pi 1} + r_{x1} + R_s}$, in

which $r_{\pi 1}$ and r_{x1} represents the base-emitter junction diffusion resistance and the series resistance in the base terminal, respectively, of transistor Q_1 .


(10 points)

- (b) In the case the input circuit produces a dominant high-frequency pole, prove

the upper 3-dB frequency ω_H is given by $\omega_H \approx \frac{1}{[r_{\pi 1} \parallel (r_{x1} + R_s)](C_{\pi 1} + 2C_{\mu 1})}$.

(10 points)

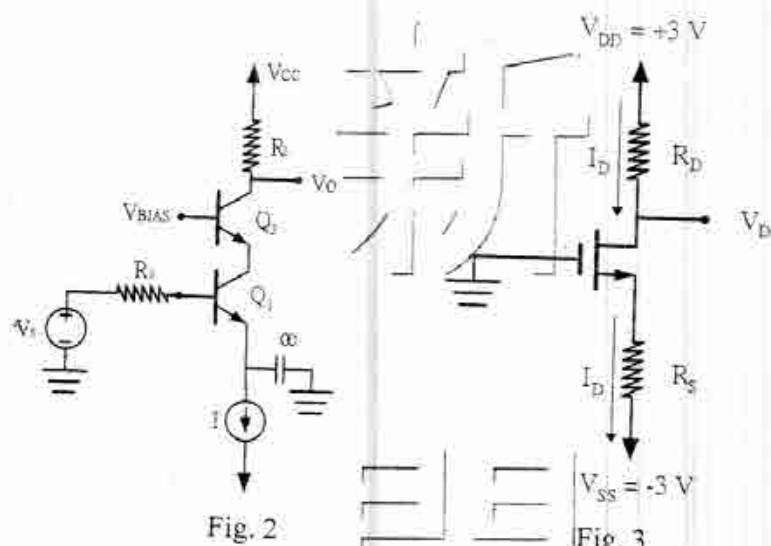- 考生注意：1. 依次序作答，只要標明題號，不必抄題。
2. 答案必須寫在答案卷上，否則不予計分，並限以藍黑色筆作答。
3. 試題隨卷繳回。(餘詳閱試場規則)



5. Design the circuit of Fig. 3 so that the transistor operates at $I_D = 0.4 \text{ mA}$ and $V_D = 1 \text{ V}$. The NMOS transistor has $V_t = 1 \text{ V}$, $\mu_n C_{ox} = 20 \mu\text{A/V}^2$, $L = 10 \mu\text{m}$, and $W = 400 \mu\text{m}$. Neglect the channel-length modulation effect. (10 points)
6. Fig. 4 shows a non-inverting op amp.
- Assume that the op amp has infinite input resistance and zero output resistance. Find an expression for the feedback factor β_f . (5 points)
 - If the open-loop voltage gain $A = 10^4$, find R_2/R_1 to obtain a closed-loop voltage gain A_f of 10. (5 points)
 - What is the amount of feedback in decibels? (5 points)
 - If A decreased by 20%, what is the corresponding decrease in A_f ? (5 points)

